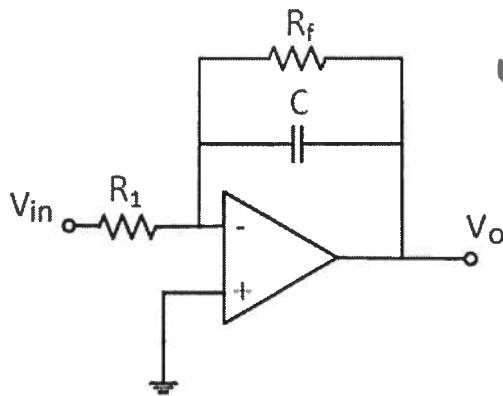


Week 3 Quiz Solutions

1. Considering the following circuit where $C=200\text{nF}$.



Lowpass Filter

$$\omega_b = \frac{1}{R_F C}$$
$$\text{gain} = \frac{-R_F}{R_1}$$
$$H(\omega) = \frac{-R_F}{R_1} \frac{1}{R_F C j\omega + 1}$$

To get a bandwidth of $\omega_b=500\text{rad/s}$ and a passband gain of -400, Determine the appropriate value of R_f and R_1 . Enter the value of R_1 in ohms


$$500 = \frac{1}{R_F (200 \times 10^{-9})} \Rightarrow R_F = \frac{1}{500 \cdot 200 \cdot 10^{-9}} = 10000 \Omega$$

$$-400 = \frac{-10000}{R_1} \Rightarrow R_1 = 25 \Omega$$

2. For the above circuit in question 1, enter the value of R_f in KILO ohms.

$$10 \text{ k}\Omega$$

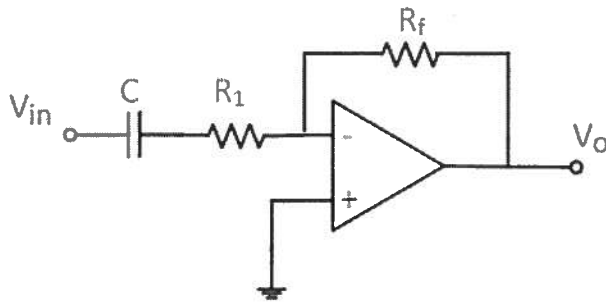3. For the following circuit, $R_1 = 100\Omega$. Select the values of R_f and C to have a passband gain of -100 and a corner frequency of 1,000 rad/s. Enter the value of C in μF .



High Pass Filter

$$H(\omega) = \frac{-R_f C j\omega}{R_1 C j\omega + 1}$$

$$\text{gain} = -\frac{R_f}{R_1}$$

$$\omega_c = \frac{1}{R_1 C}$$

$$1000 = \frac{1}{100 C}$$

$$\Rightarrow C = 1 \times 10^{-5} \text{ F} \\ = 10 \mu\text{F}$$

4. From the above circuit in question 3, enter the value of the value of R_f in $\text{k}\Omega$.

$$-100 = \frac{-R_f}{100} \Rightarrow R_f = 10 \text{ k}\Omega$$

5. What is the DC gain of a filter circuit that has the given transfer function?

$$H(\omega) = \frac{10}{j\omega + 5}$$

$$\text{DC gain} = |H(\omega)| \text{ for } \omega = 0$$

$$\frac{10}{j0 + 5} = \boxed{2}$$

6. What is the bandwidth in radians-per-second of a filter circuit that has the given transfer function?

$$H(\omega) = \frac{10}{j\omega + 5}$$


Rewrite as

$$\frac{10}{5} \frac{1}{j\omega \frac{1}{5} + 1}$$

\Rightarrow Low pass filter with gain of 2 and bandwidth of $\boxed{\frac{5 \text{ rad}}{\text{s}}}$

$$2 \frac{1}{j\frac{\omega}{5} + 1}$$

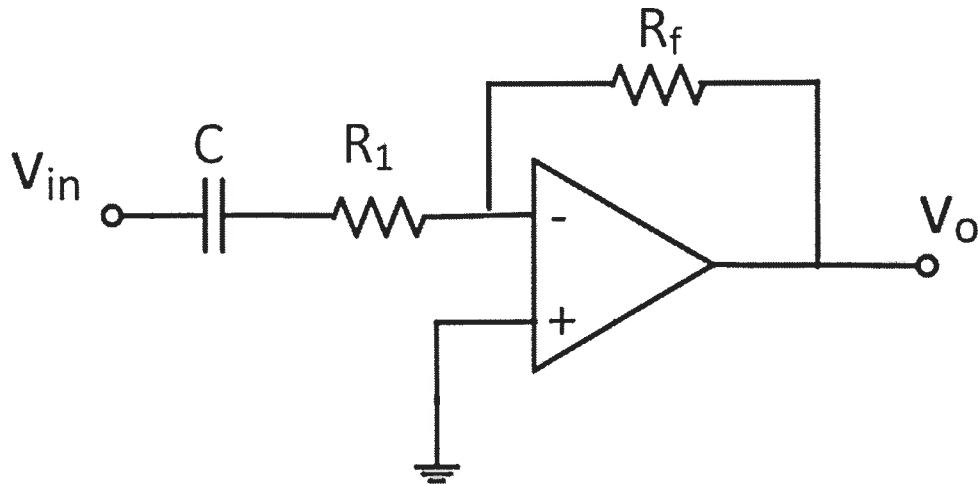7. A sine wave with amplitude 2 V and frequency 1358 Hz is applied to the circuit shown. If $R_f = 10 \text{ k}\Omega$, $R_1 = 1.5 \text{ k}\Omega$, and $C = 0.1 \text{ }\mu\text{F}$, what is the amplitude of the output sine wave?



High pass filter

$$H(f) = -\frac{R_f}{R_1} \frac{j\frac{f}{f_0}}{j\frac{f}{f_0} + 1}$$

$$|H(1358)| = \left| -\frac{10}{1.5} \frac{j\frac{1358}{1061.03}}{j\frac{1358}{1061.03} + 1} \right|$$

$$= 6.6667 \frac{1358/1061.03}{\sqrt{1^2 + \left(\frac{1358}{1061.03}\right)^2}} = 6.6667 \frac{1.2799}{1.6242}$$


$$V_o = V_{in} \times \text{Gain} = 2 \times 5.25 = \boxed{10.5 \text{ V}}$$

$$f_0 = \frac{1}{2\pi R_1 C}$$

$$= \frac{1}{2\pi \cdot 1500 \cdot 0.1 \times 10^{-6}}$$

$$= 1061.03 \text{ Hz}$$

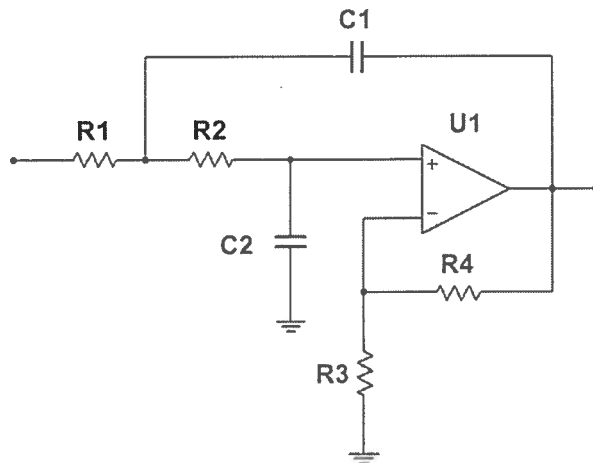8. In the filter circuit shown, $R_1 = 10\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_3 = 4\text{k}\Omega$, $R_4 = 6.8\text{k}\Omega$, $C_1 = 5.3\text{nF}$, and $C_2 = 5.3\text{nF}$. $1\text{ nF} = 1\text{ nanofarad} = 10^{-9}\text{ farads}$. What is the midband gain of this filter? Calculate your answer to at least the nearest tenth.



Sallen-Key Low Pass

$$K = 1 + \frac{R_4}{R_3} = 1 + \frac{6.8}{4} = \boxed{2.7}$$

9. For the above circuit in question 8, what is the resonance frequency in kilohertz? Calculate your answer to at least the nearest tenth.

$$f_0 = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}} = \boxed{3.0\text{ kHz}}$$

10. For the above circuit in question 8, what is the quality factor? Calculate your answer to at least the nearest tenth.


Since $R_1 = R_2 = R$ + $C_1 = C_2 = C$

$$K = 3 - \frac{1}{Q} \Rightarrow \frac{1}{Q} = 3 - 2.7 = 0.3$$

$$\boxed{Q = 3.3}$$

OR CAN USE $Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(1-K)R_1 C_1 + (R_1 + R_2)C_2}$

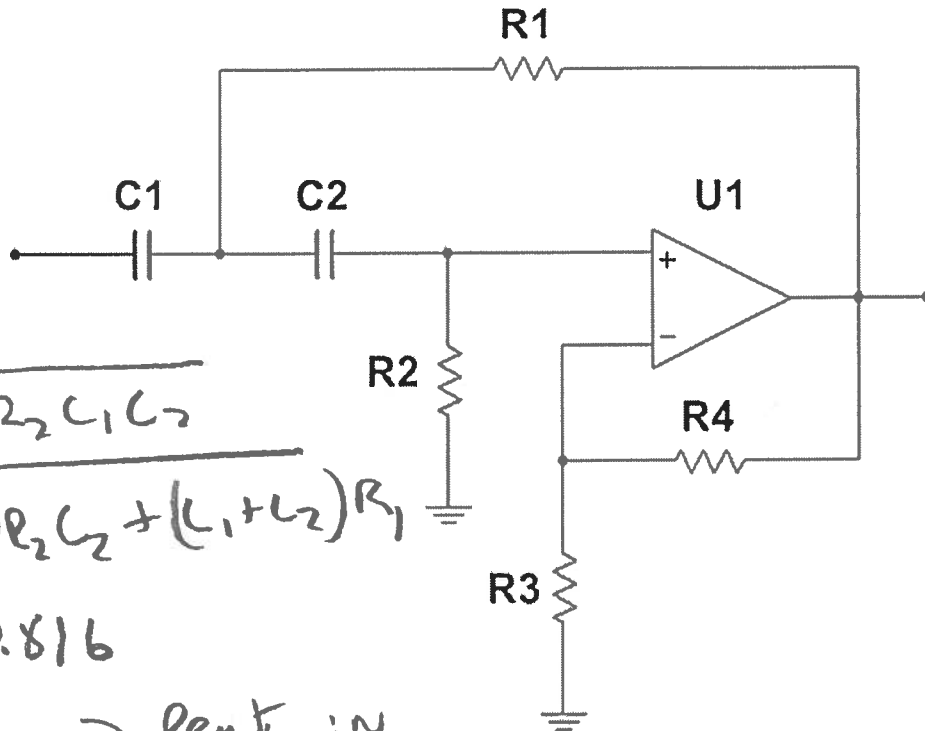11. In the filter circuit shown, $R_1 = 10\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_4 = 2\text{k}\Omega$, $C_1 = 0.15\text{ }\mu\text{F}$, and $C_2 = 0.1\text{ }\mu\text{F}$. $1\text{ }\mu\text{F} = 1\text{ microfarad} = 10^{-6}\text{ farads}$. Which of the following are not true for the circuit shown.



$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(1-K) R_2 C_2 + (C_1 + C_2) R_1}$$

$$= 0.816$$

$> \frac{1}{\sqrt{2}} \Rightarrow$ peak in magnitude of transfer function

T ☒ There is a peak in the transfer function of this filter.

F ☒ The DC gain is 2

$$1 + \frac{R_4}{R_3} = 1 + \frac{2}{2} = 2 = \text{pass band gain, NOT DC gain.}$$

T ☒ The resonance frequency increases as the value of C_2 is decreased.

F ☒ The resonance frequency is approximately 130 radians per second.

$$\hookrightarrow \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}} = 129.9 \text{ Hz (Not rad/s)}$$

$$f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}} \quad C_2 \downarrow \Rightarrow f_0 \uparrow$$