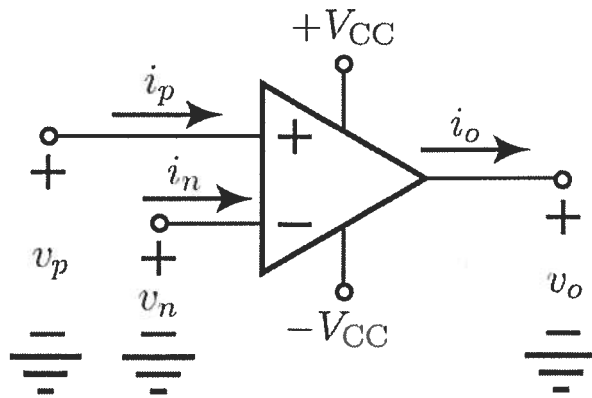


Week 2 Quiz Solutions


1.



For the ideal operational amplifier circuit above, which of the following are true?

- ☒ $i_p = i_n$
- ☒ $i_n = 0$
- ☐ $v_p / i_p = 0$
- ☒ $v_o \leq V_{CC}$


2.

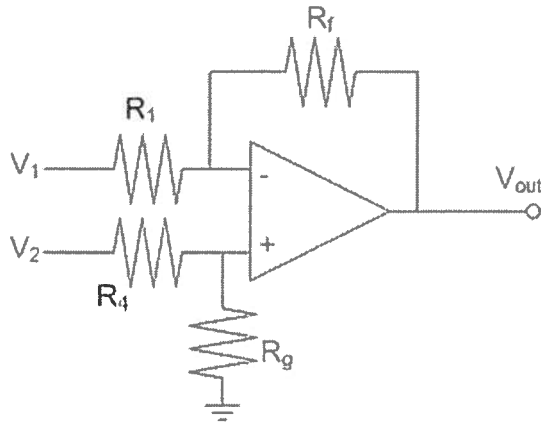

For the difference amplifier circuit above, if $R_1 = R_4 = 1000\Omega$ and $R_f = R_g = 2000\Omega$, what is the gain, G , of the circuit where $v_o = G(v_2 - v_1)$?

$$G = \frac{R_f}{R_1} = \frac{2000}{1000} = 2$$

3.

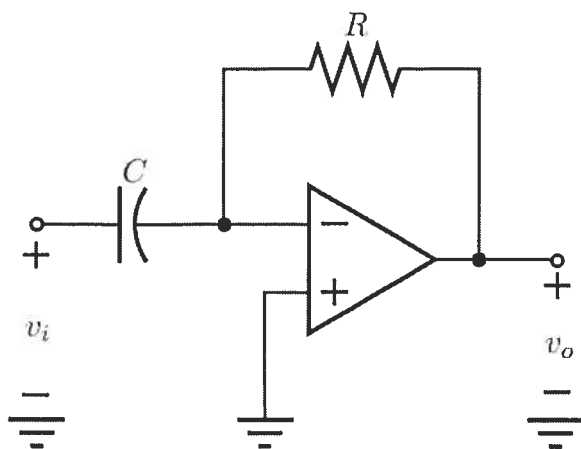

Consider the inverting differentiator shown above. If $R=2000\Omega$ and $C=0.25\mu\text{F}$, and $V_i(t)=e^{-2000t}\text{V}$ what is the accurate expression for $V_o(t)$?

☐ $V_{out}(t)=2000e^{-2000t}\text{V}$

☐ $V_{out}(t)=.005e^{-2000t}\text{V}$

☒ $V_{out}(t)=e^{-2000t}\text{V}$

☐ $V_{out}(t)=-2000e^{-2000t}\text{V}$


$$V_o = -RC \frac{dV_i}{dt}$$

$$= -(2000 \cdot 0.25 \times 10^{-6}) \frac{dV_i}{dt}$$

$$= -0.5 \times 10^{-3} (-2000) e^{-2000t}$$

$$= e^{-2000t} \checkmark$$

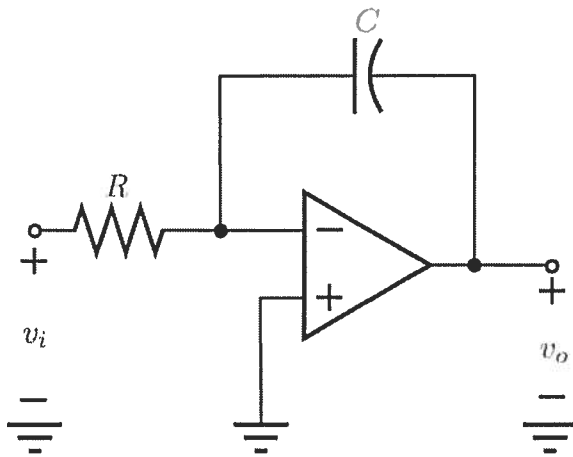4. The input to the following op amp circuit is $v_i(t) = 10\cos(100t)$. If $R = 10\text{k}\Omega$ and $C = 2\mu\text{F}$, determine the value of v_o in volts and select the most appropriate answer below.



- ☐ $v_o(t) = 50\cos(100t)$.
- ☐ $v_o(t) = -10\cos(100t)$.
- ☒ $v_o(t) = 5\cos(100t + 90^\circ)$.
- ☐ $v_o(t) = 5\cos(100t)$.
- ☐ $v_o(t) = 5\cos(100t - 90^\circ)$.

$$V_o = \frac{-1}{RC} \int_0^t v_{in} dt$$


$$= \frac{-1}{2 \times 10^{-2}} \frac{10}{100} \sin(100t)$$

$$= -5 \sin 100t$$

$$\sin x = \cos(x - 90^\circ) = -\cos(x + 90^\circ)$$

$$-5 \sin(100t) = 5 \cos(100t + 90^\circ)$$

5.

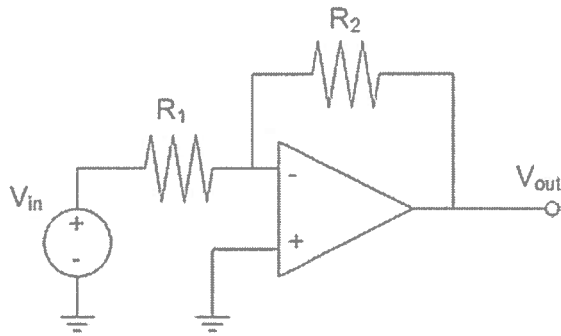


For the inverting operational amplifier circuit above, if $R_2 = 10\text{k}\Omega$ and the closed-loop gain is $G = -5000$, what is the appropriate resistance for R_1 ? Submit your answer in units of Ohms, while omitting the unit. For example, if your answer is 1000Ω submit 1000.

$$G = -\frac{R_2}{R_1} \Rightarrow -5000 = -\frac{10000}{R_1}$$

$$R_1 = \frac{10000}{5000} = 2\Omega$$



6.

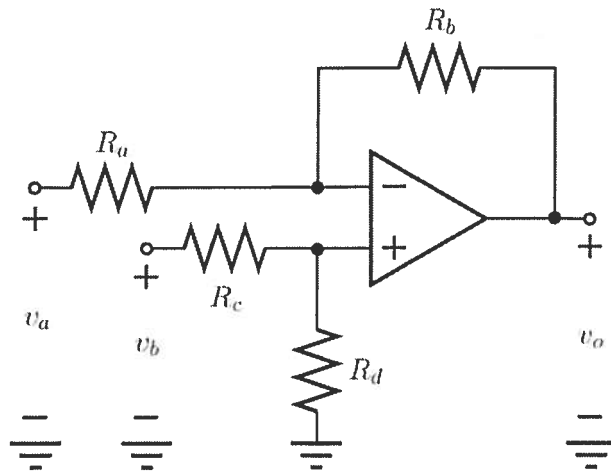

For this question, $R_a=3\text{k}\Omega$, $R_b=12\text{k}\Omega$, $R_c=3\text{k}\Omega$, and $R_d=12\text{k}\Omega$. $v_a=6\text{V}$ and $v_b=14\text{V}$. What is v_o ? Give your answer in Volts and omit the units from your answer.


$$v_o = \frac{R_b}{R_a} (v_b - v_a) = \frac{12}{3} (14 - 6) = 4(8) = 32\text{V}$$

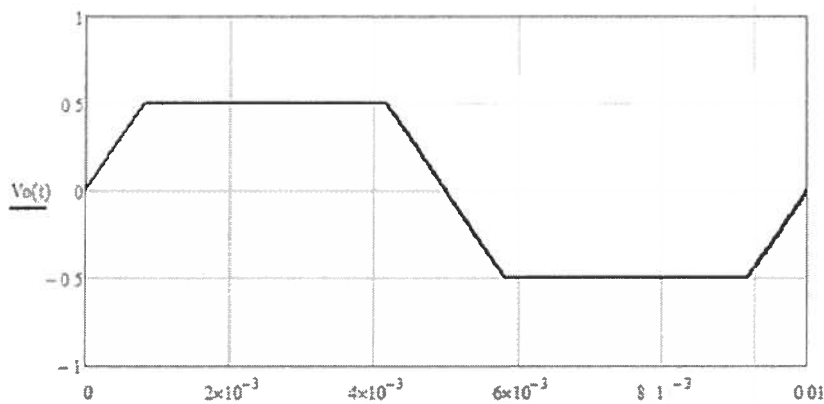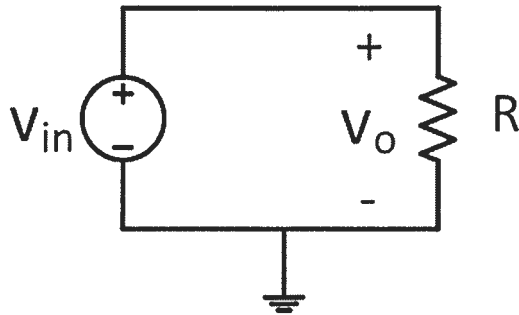7. For the circuit shown, $V_{in} = V_{in}(t) = \sin(\omega t)$ and $R = 100\Omega$. A plot of the output voltage $V_O(t)$ is shown. What is the maximum current in milliamps that can be supplied by the voltage source?



$$\begin{aligned} \text{Maximum current} &= \frac{\text{Max Voltage}}{R} \\ &= \frac{0.5 \text{ V (from plot)}}{100} = 0.005 \text{ A} \\ &= 5 \text{ mA} \end{aligned}$$

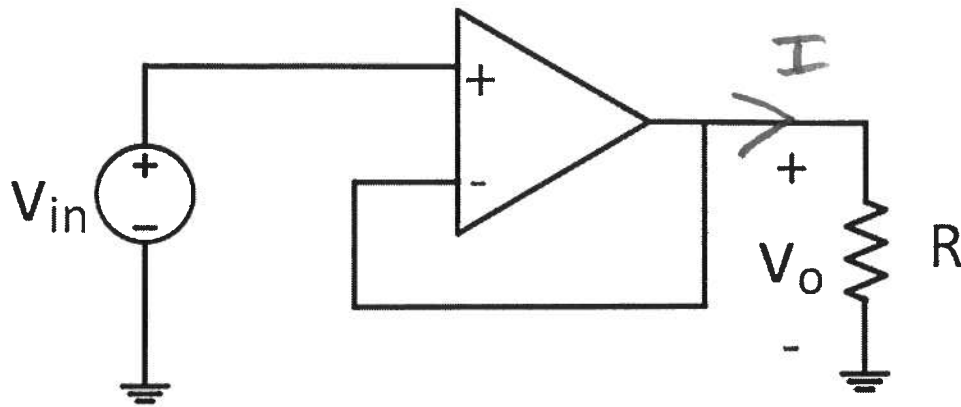8. An opamp is used as a buffer between the source and the load resistor R in the circuit of question 7 as shown. What minimum current in milliamps must the op-amp be able to supply so that $V_O(t) = V_{in}(t)$?




I is a maximum when V_{in} is a max of $1V$.

$$I = \frac{1V}{100\Omega} = 10mA.$$

The op amp must be able to supply at least this current or the output will be clipped for the $1V$ amplitude sine wave input.

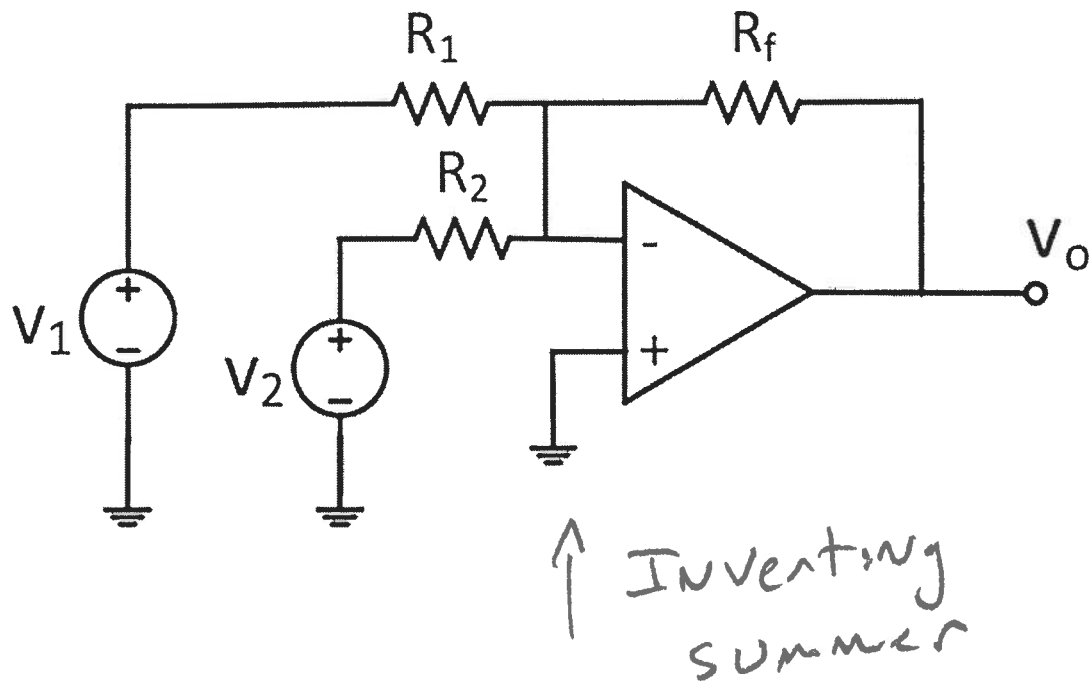9. For the circuit shown, $V_1 = 3V$, $V_2 = -2V$, $R_1 = 2k\Omega$, $R_f = 10k\Omega$, and the output voltage $V_O = -7V$. What is the value of the resistor R_2 in $k\Omega$?



$$V_O = -\frac{R_f}{R_1} V_1 + -\frac{R_f}{R_2} V_2$$

$$-7 = -\frac{10}{2} 3 + -\frac{10}{R_2} (-2)$$

$$8 = \frac{20}{R_2} \Rightarrow R_2 = \frac{20}{8} = 2.5 k\Omega$$